
Homework Assignment 2 – Review of Laplace transform

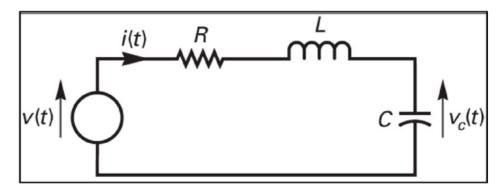- 1) Complete the proof of the convolution property for the Laplace transform
- 2) Consider the following circuit:



- a. Find the differential equation relating the input v(t) to output $v_c(t)$.
- b. Defining the parameters: $\omega_0 = \frac{1}{\sqrt{LC}}$ and $\varsigma = \frac{R}{2} \sqrt{\frac{C}{L}}$ (the natural frequency and damping).

Find the transfer function for this system in terms of $\, \varpi_{\! 0} \,$ and $\, arsigma \,$

Find the pole-zero map, impulse response, and step response for the following values of $\, \varpi_{\! 0} \,$ and $\, arsigma \,$

- c. $\omega_0 = 4$ and $\varsigma = 0.25$
- d. $\omega_0 = 4$ and $\varsigma = 0.025$
- e. $\omega_0 = 8$ and $\varsigma = 0.25$
- 3) Consider the following transfer function: $X(s) = \frac{s+2}{(s+2)^2+1}$
 - a. Find the corresponding differential equation.
 - b. Find the pole-zero map, impulse response, and step response.